

circuits rarely use the highest-quality capacitors because of space limitations. You can design the impedance converter without dc-blocking capacitors.

**Figure 1** shows the self-balanced impedance converter. The self-polarized electret condenser-microphone capsule,  $X_1$ , connects to the high-impedance gate of JFET  $Q_1$ .  $Q_2$ , an ac-current source, loads source follower  $Q_1$ .  $Q_2$ , thanks to  $C_2$ , has high impedance but allows a fixed dc voltage on the  $Q_1$  source.

The circuit sources phantom power at 48V dc through  $R_{PH1}$  and  $R_{PH2}$  at the mixing-console end of the microphone cable.  $Q_2$ 's emitter drives—and  $R_{PH1}$  loads—emitter follower  $Q_3$ . The signal from  $Q_3$ 's emitter bootstraps the


**TABLE 1 PERFORMANCE PARAMETERS**

Mixing-console input impedance $R_{IN}$ (k $\Omega$ )	Peak input clipping voltage (V)	Input voltage at –80-dB (0.01%) distortion
1.2	3.1	140 mV rms
2.4	5.8	750 mV rms
10	13.6	3.1V rms

drain of  $Q_1$ , reducing the ac voltage across the gate-to-drain capacitance and resulting in lower input capacitance at the gate of  $Q_1$ .  $R_{PH2}$  supplies current for shunt-regulator-voltage sources  $D_2$  and  $Q_4$ .  $R_4$  and  $C_4$  attenuate zener-diode noise. Integrator  $IC_1$  compares the dc voltages on the XLR connector's pins 2 and 3 and, through  $Q_2$  and  $Q_3$ , maintains a difference

**TABLE 2 PERFORMANCE PARAMETERS FOR JFETs**

$Q_1$ part	A-weighted noise voltage ( $\mu$ V rms)
2SK596	4
2SK660	3.6
2SK2219	4.1
TF202C	4.6

 

**Figure 2** The voltage-noise density versus frequency for the circuit of **Figure 1** varies with different types of input JFET  $Q_1$ . The source impedance of  $X_1$  is 10 pF.

equal to the op amp's input offset voltage. Thus, if the microphone input at the mixer console is transformer-coupled, both ends of its winding are at the same voltage. No dc will flow through the winding and saturate the core.  $IC_1$  should have a common-mode-input-voltage range equal to that of the positive-supply rail. You can accomplish this task using, for example, an op amp with a P-channel JFET input stage. **Tables 1** and **2** and **Figure 2** show typical performance parameters for the impedance converter in **Figure 1**. **EDN**

## REFERENCE

1 Gaskell, Robert-Eric, "Capacitor 'Sound' in Microphone Preamplifier DC Blocking and HPF Applications: Comparing Measurements to Listening Tests," Audio Engineering Society, Presentation 130, Paper 8350, May 2011, pg 1, <http://bit.ly/zVcgtc>.

## Simple sawtooth generator operates at high frequency


Luca Bruno, IIS Henseberger Monza, Lissone, Italy

**➡** Pulse-width-modulation signal-generator circuits often use an analog sawtooth-oscillator function, but it also can be useful in other applica-

tions. The inexpensive sawtooth generator in **Figure 1** suits use in low-power applications operating at frequencies as high as 10 MHz and beyond and

those in which ramp linearity and frequency accuracy are not prominent concerns.

The circuit employs a single Schmitt-trigger inverter, which acts as a modified astable multivibrator. The output waveform is the voltage across timing capacitor  $C_T$ , which ramps between the lower and the upper threshold voltages of the

 

**Figure 1** You can use the  $C_T$  ramp's charge and fast discharge to produce a sawtooth. The upper and lower trip-point voltages of the Schmitt trigger limit the sawtooth. See text for the values of  $V_{CC}$ ,  $C_T$ , and  $R_T$ .

## TO IMPROVE FREQUENCY ACCURACY, USE A FAST LOGIC FAMILY WITH LOW PROPAGATION DELAY AND HIGH OUTPUT CURRENT.

inverter. Charging the  $R_T C_T$  network at constant voltage causes the ramp, so its response is exponential, approximately linear only for the initial part of the exponential rise.

A simple trick to improve ramp linearity is to charge the  $R_T C_T$  network with a higher-voltage source. Capacitor  $C_1$ , which has a value that is at least 10 times greater than that of  $C_T$ , acts as a charge pump. When the gate output is low during the falling edge of the sawtooth, capacitor  $C_1$  quickly charges through diode  $D_1$  to  $V_{CC}$  minus the for-

ward voltage of  $D_1$ . Meanwhile, capacitor  $C_T$  discharges quickly through diode  $D_2$ .

When the falling  $C_T$  voltage reaches the Schmitt trigger's lower trip point,  $V_{T-}$ , the gate output returns high. The charge on  $C_1$  drives the cathode of  $D_1$  to the sum of the voltage of capacitor  $C_1$  and the gate's high output voltage.  $D_1$  becomes reverse-biased, and the  $R_T C_T$  network begins to charge to the voltage on  $C_1$ , along with the gate's high output voltage. When  $C_T$  reaches the Schmitt trigger's upper trip point,  $V_{T+}$ , the gate's output returns low, and the cycle repeats.

Ramp linearity is proportional to the sum of the  $V_{CC}$  and  $V_{DD}$  supply voltages. Because  $V_{DD}$  is fixed at 5V, you can improve ramp linearity if  $V_{CC}$  can assume a value higher than that of the inverter. You can estimate the ramp's nonlinearity error using the following equation:

$$E_{NL}\% = \left( \frac{M_I - M_F}{M_I} \right) 100,$$

where  $E_{NL}\%$  is the percentage of nonlinearity error,  $M_I$  is the initial slope of the ramp, and  $M_F$  is the final slope of the ramp, and

$$E_{NL}\% = \left( \frac{V_{T-}^+ - V_{T-}^-}{V_{CC} + V_{DD} - V_F - V_{T-}^-} \right) 100,$$

where  $V_F$  is the forward-voltage drop across  $D_1$ .

The  $R_T C_T$  time constant sets the frequency,  $F_O$ , of the sawtooth signal. You can estimate the frequency by applying a simple model to the circuit, which neglects the discharge time of  $C_T$  and any discharge of  $C_1$ , yielding

the following equation:

$$F_O = \frac{1}{K R_T C_T},$$

where  $K$  is a constant, which the following equation defines:

$$K = \ln \left( \frac{V_{CC} + V_{DD} - V_F - V_{T-}^-}{V_{CC} + V_{DD} - V_F - V_{T-}^+} \right).$$

By simulating the circuit with  $C_T = 100$  pF and  $R_T = 2.2$  k $\Omega$ , which agree with the values that the equations theoretically calculated, you can obtain ramp-nonlinearity errors of 28% with both  $V_{CC}$  and  $V_{DD}$  equal to 5V, 18% with  $V_{CC}$  of 10V and  $V_{DD}$  of 5V, and 14% with  $V_{CC}$  of 15V and  $V_{DD}$  of 5V.

The breadboarded circuit has  $V_{DD} = V_{CC} = 5V$ ,  $C_T = 100$  pF, and  $R_T = 2.2$  k $\Omega$ . IC<sub>1</sub> is a standard dual-in-line, eight-pin 74HC14, which has a maximum propagation delay of 15 nsec versus 4.4 nsec for the SN74LVC1G14 inverter with a  $V_{DD}$  of 5V. The frequency is approximately 12.7 MHz.

$C_T$  should be a low-leakage film capacitor, and its value should be kept low to reduce its charging and discharging of a large amount of energy. Select  $C_T$  with a large enough value compared with the gate's input capacitance and unwanted stray capacitances so that they do not introduce a significant error. Select  $R_T$  with a small enough value that the load impedance, gate input, and stray capacitances do not introduce significant error. You can use any CMOS Schmitt-trigger inverter to test the circuit. To improve frequency accuracy, however, you should use a fast logic family with low propagation delay and high output current, such as the single-gate SN74LVC1G14 from Texas Instruments.

You should measure the threshold trigger voltages, especially  $V_{T-}$ , directly from the circuit under test before using the preceding equations. Quickly discharging  $C_T$  to ground through a finite-propagation-delay inverter causes the lower limit of the ramp to reset below the lower threshold,  $V_{T-}$ . You can compensate for the resulting error if you use the measured value of  $V_{T-}$ , which takes this effect into account. **EDN**